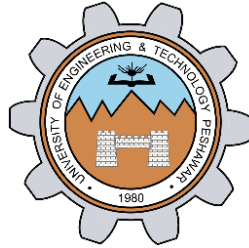


# **MICROPROCESSOR BASED SYSTEM DESIGN**

## **TASK 10**



**Spring 2021**

**CSE307 MBSD**

Submitted by: **Shah Raza**

Registration No. : **18PWCSE1658**

Class Section: **B**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Student Signature: \_\_\_\_\_

Submitted to:

**Dr. Bilal Habib**

Sunday, July 11, 2021

**Department of Computer Systems Engineering**  
**University of Engineering and Technology, Peshawar**

## Task:

In this project you are required to interface an ADC and DAC, to 89C51 microcontroller as shown below in figure 1.


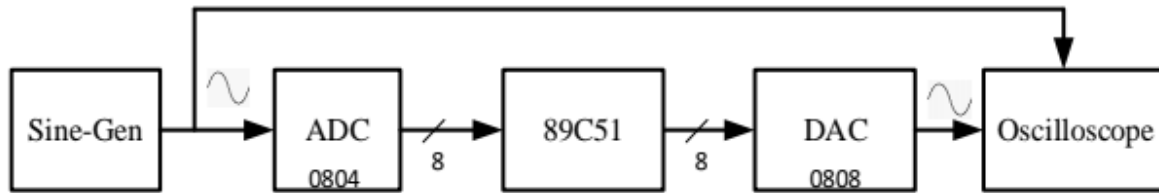


Figure 1: ADC and DAC interfaced to Microcontroller

Show the original sine wave and the final output of DAC on the oscilloscope as shown in figure 1. If you see any distortions in the DAC output, clean them using filters. Written report must have answers of the questions below,

- **Input signal to ADC has a frequency ( $f_{in}$ ) of 100Hz. How you supplied it.**

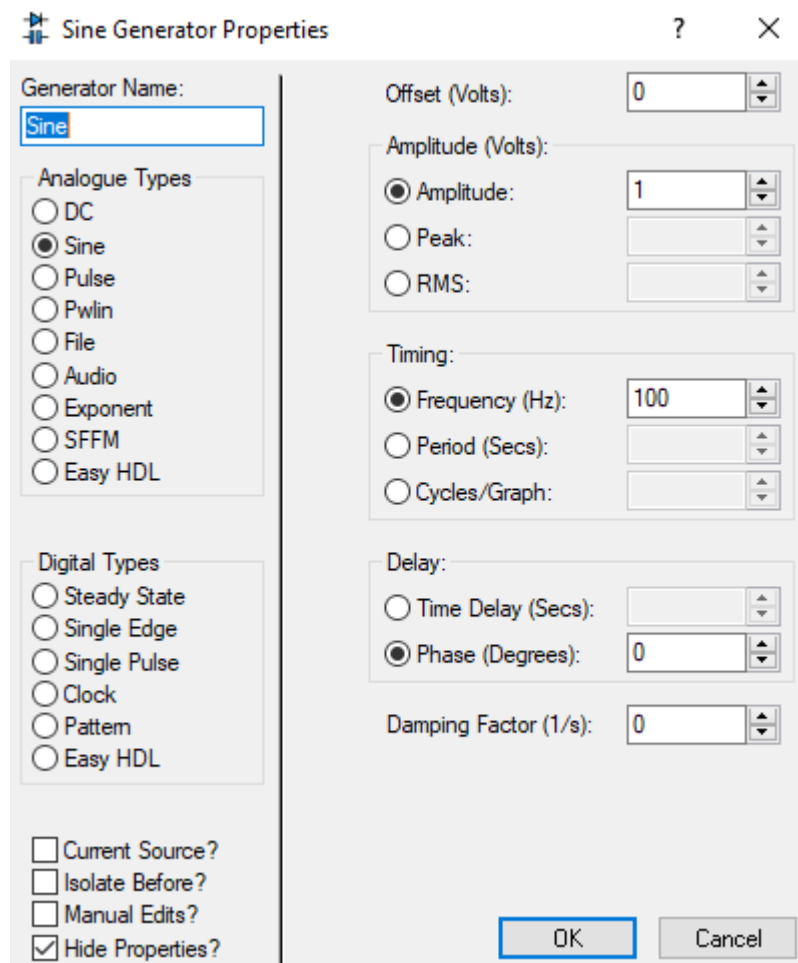
**Answer:** I supplied this input frequency by editing the properties of sine generator.




- What happens if you decrease the sampling rate ( $f_s$ ) from 1K, 0.5K to 0.2K samples per second?

**Answer:** If we decrease the sampling rate from 1k to 0.5K and then to 0.2K, the output signal will be distorted as we are not taking enough samples to reform the original signal.

**Output Signal ( $f_s = 0.5K$ ):**

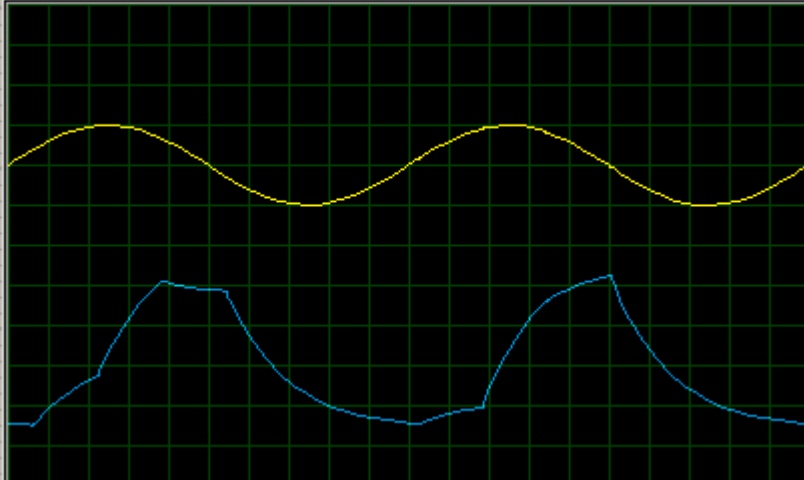

**Output Signal ( $f_s = 0.2K$ ):**

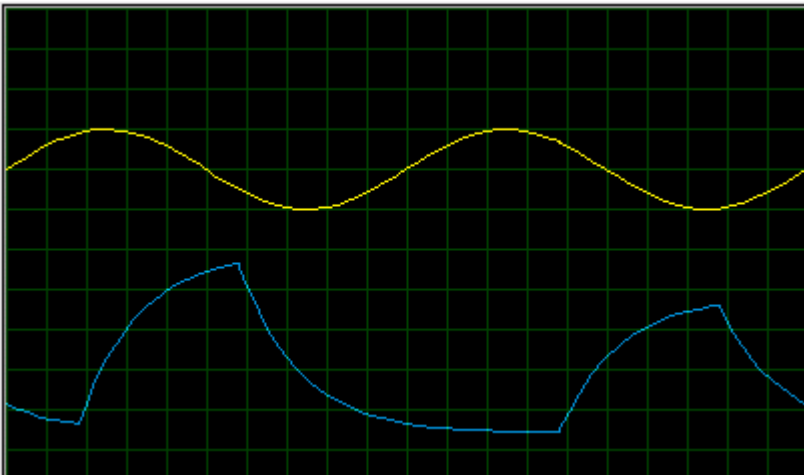

- What reference voltage ( $V_{ref}$ ) has been used for ADC?

**Answer:** I have used 1V reference voltage for ADC in this task. I did this by supplying 0.5V at the  $V_{ref}/2$  Pin of the ADC.

- What is the relationship of  $V_{ref}$  to the amplitude of input signal.

**Answer:** The amplitude of input signal varies directly with the reference voltage. For example if  $V_{ref} = 3V$  then we can supply an input signal with an amplitude of 3V.

- What will be the step-size?

**Answer:** We know that Step-size =  $V_{in}/2^n$

So step-size =  $1V/2^8 = 1V/256 = 3.90mV$

- **What is the input voltage range of ADC?**

**Answer:** As my reference voltage is 1V so, the input voltage range of my ADC is 0V -1V.

- **Can we increase the frequency of input signal ( $f_{in}$ ) to 10KHz, if not then why?**

**Answer:** No, we cannot increase the frequency of input signal to 10KHz because we will need a sampling frequency of 1MHz for that, which is practically not possible to achieve.

- **What is the limit of DAC, how fast it can work?**

**Answer:** Number of DAC outputs =  $2^n = 2^8 = 256$ .

The setting time of DAC is 150 ns which is very fast.

- **Use Low pass RC filter to clean the output of DAC. Find the optimal values of R and C in this filter.**

**Answer:** The input signal frequency is 100Hz and we are using low pass filter, so to block signals of frequency greater than 100Hz our cut-off frequency should be 100Hz.

$$F_c = 1/(2\pi RC)$$

$$100\text{Hz} = 1/(2\pi RC)$$

$$RC = 1/(2\pi \cdot 100) = 0.00159$$

If we take  $R = 1\text{K ohm}$  then

$$C = 0.00159/1000 = 1.59 \mu\text{F}$$

### Code:

```
#include <reg51.h>
```

```
#include <stdio.h>
```

```
sbit RD_n = P3^0; //P3.0 is connected to the RD pin of ADC
```

```
sbit WR_n = P3^1; //P3.1 is connected to the WR pin of ADC
```

```
sbit INTR = P3^2; //P3.2 is connected to the INTR pin of ADC
```

```
void Ext0(void); //Function that is called after the ADC is done with conversion
```

```
void main(void)
```

```
{
```

```
    P2 = 0xFF; //Set P2 as an input Port
```

```
    P1 = 0x00; //Set P1 as an output Port
```

```
    INTR = 1; //Set P3.2 as an input pin
```

```
    while (1)
```

```
    {
```

```
        RD_n = 1; //Set the RD pin to High
```

```
        WR_n = 0; //WR = Low
```

```
        WR_n = 1; //Low-->High
```

```
        while(INTR==1); //Wait for the ADC to Convert the given voltage
```


```
        Ext0(); //Call the Ext0 function
```

```
    }
```

```
void Ext0()
{
    RD_n = 0; //Set the RD pin of ADC from HIGH to LOW
    //The ADC sends the converted value to P2
    P1 = P2; //Send the value at P2 to P1
}
```

### Output / Graphs / Plots / Results:

**Schematic:**

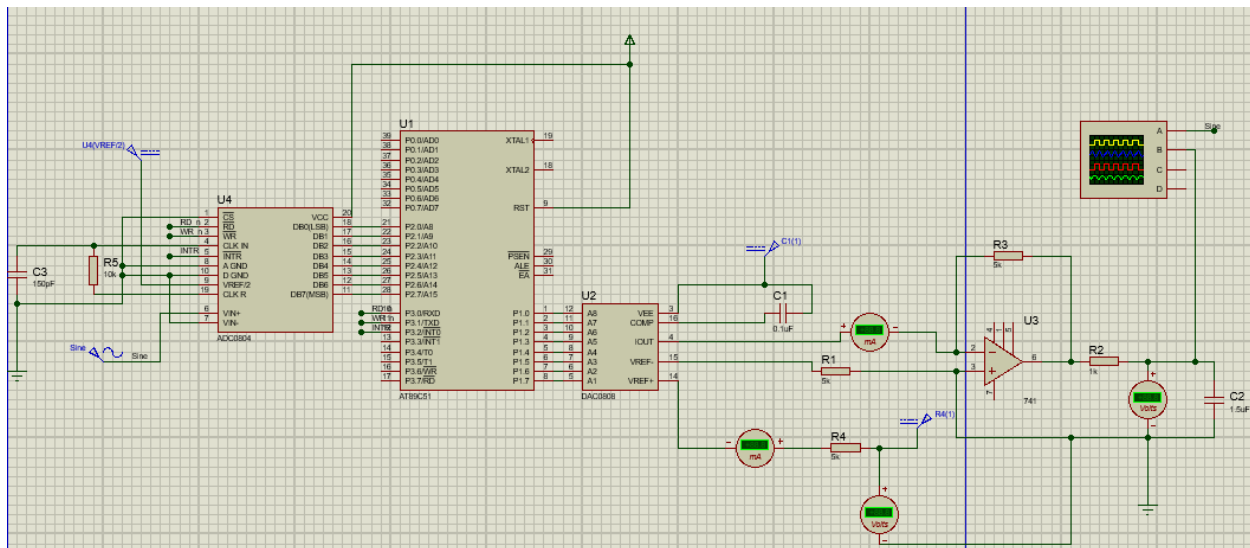

### Oscilloscope Output:

## Digital Oscilloscope

