

# **DIGITAL SYSTEM DESIGN LAB**

**LAB #06**



**Spring 2021**

**CSE308L DSD LAB**

Submitted by: **Shah Raza**

Registration No. : **18PWCSE1658**

Class Section: **B**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Student Signature: \_\_\_\_\_

Submitted to:

**Engr. Madiha Sher**

Monday, June 14, 2021

**Department of Computer Systems Engineering**  
**University of Engineering and Technology, Peshawar**

## Objectives:

This lab will enable students to:


- Code using Behavioral level modeling
- Implement FSM of BCD Counter

## Task # 01:

Develop a verilog model for the FSM of BCD Counter (0 – 9), which rolls over when it reaches 9 to 0.

## Problem Analysis:

### State Diagram:

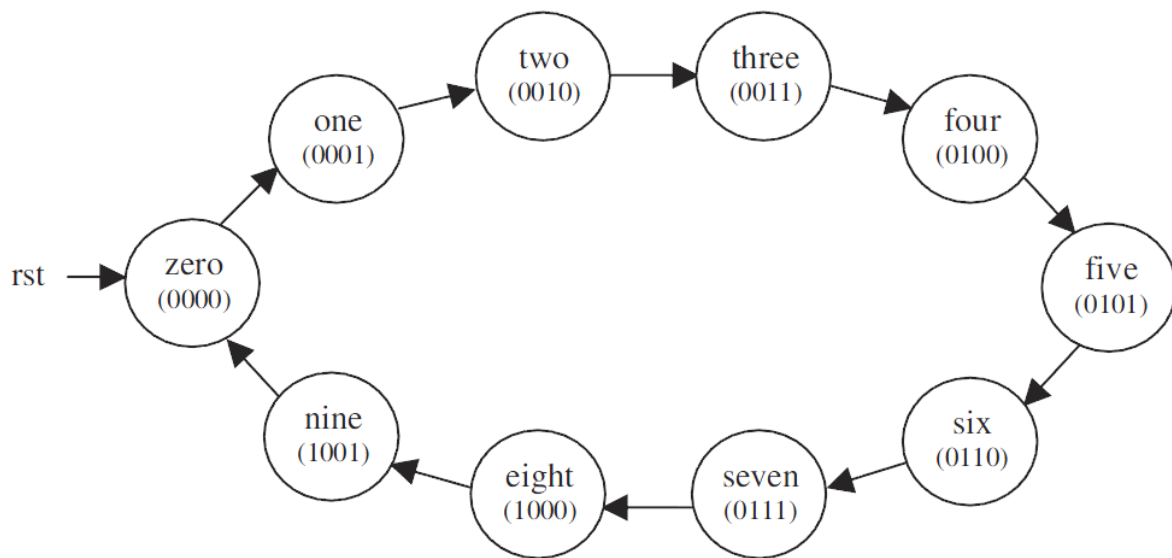

## Code:

### BCD Counter:

```
module BCD_Counter(reset,clk,out);
    input reset,clk;
    output [3:0] out;
    reg [3:0] out;

    reg [3:0] state, next_state;

    always @(posedge clk)
        state = next_state;

    always @(state or reset)
        begin
```

```

        if(reset)
            next_state = 4'b0000;
        else
            next_state <= (state<9)?(state+1):4'b0000;
        out = next_state;
    end

endmodule

```

### **TestBench:**

```

module testBench;
    reg clk, reset;
    wire [3:0] out;

    BCD_Counter c1(reset,clk,out);

    always
        #2 clk = ~clk;

    initial
    begin
        clk =0;
        reset = 1;
        $display("reset   out");
        $monitor("%b    %b",reset,out);
        #4
        reset = 0;
        #200 $stop;
    end


endmodule

```

## Output:

```
# reset out
# 1 0000
# 0 0000
# 0 0001
# 0 0010
# 0 0011
# 0 0100
# 0 0101
# 0 0110
# 0 0111
# 0 1000
# 0 1001
# 0 0000
# 0 0001
# 0 0010
# 0 0011
# 0 0100
# 0 0101
# 0 0110
# 0 0111
# 0 1000
# 0 1001
# 0 0000
# 0 0001
# 0 0010
# 0 0011
# 0 0100
```

## Waveform:

 

## Dataflow:

