 



Problem 1: Draw the logic circuit described by the Verilog code below.

```
module AEqualsB (A1, A0, B1, B0, F);  
    input A1, A0, B1, B0;  
    output F;  
    wire w1, w2;  
    and a1 (F, w1, w2);  
    xnor x1 (w1, A1, B1);  
    xnor x2 (w2, A0, B0);  
endmodule
```

Solution:



 Problem 2: Write a Verilog explicit structural description of the following logic.



Solution:

```
module Quiz1_q2 (A, B, C, D, F);  
    input A, B, C, D;  
    output F;  
    wire t1, t2, t3, t4;  
    and a1 (t1, A, B);  
    not n1 (t2, C);  
    or o1 (t3, t1, t2);  
    and a2 (t4, t3, D);  
    not n2 (F, t4);  
endmodule
```