

DIGITAL SYSTEM DESIGN LAB

LAB #09



Spring 2021

CSE308L DSD LAB

Submitted by: **Shah Raza**

Registration No. : **18PWCSE1658**

Class Section: **B**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Student Signature: _____

Submitted to:

Engr. Madiha Sher

Saturday, July 10, 2021

Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar

Task # 01:

Implement 4-bit binary counter and display the result on LEDs and 7-segment display.

Code:

Counter:

```

module Counter(clk,rst,dp,out,count);
    input clk,rst;
    output [6:0] out;
    output dp;
    output reg [3:0] count = 0;
    wire oclk;

    BINARYto7SEG c1(count,out,dp);

    Divider d1(clk,oclk,rst);

    always @(posedge oclk)
        if(rst==0)
            count =0;
        else
            count = count + 1;

endmodule

```

Divider:

```

module Divider(input iclk,output reg oclk,input rst);
    reg [100:0] count;
    always @(posedge iclk)
        if(rst==0)
            begin
                oclk = 0;
                count = 0;
            end
        else
            begin
                count = count+1;
                if(count==100000000)
                    begin
                        oclk = ~oclk;
                        count = 0;
                    end
            end
        end
    end
endmodule

```

BINARYto7SEG:

```
module BINARYto7SEG (A, Out, Dp);
```

```
    input [3:0] A;
```

```
    output [6:0] Out;
```

```
    output Dp;
```

```
    assign {Dp,Out} = (A==4'b0000)?(8'b00000001):
```

```
        (A==4'b0001)?(8'b01001111):
```

```
        (A==4'b0010)?(8'b00010010):
```

```
        (A==4'b0011)?(8'b00000110):
```

```
        (A==4'b0100)?(8'b01001100):
```

```
        (A==4'b0101)?(8'b00100100):
```

```
        (A==4'b0110)?(8'b00100000):
```

```
        (A==4'b0111)?(8'b00001111):
```

```
        (A==4'b1000)?(8'b00000000):
```

```
        (A==4'b1001)?(8'b00000100):
```

```
        (A==4'b1010)?(8'b00001000):
```

```
        (A==4'b1011)?(8'b01100000):
```

```
        (A==4'b1100)?(8'b00110001):
```

```
        (A==4'b1101)?(8'b01000010):
```

```
        (A==4'b1110)?(8'b00110000):
```

```
        (A==4'b1111)?(8'b00111000); (8'b10000000);
```

```
endmodule
```

UCF File:

```
net "rst" LOC =m18 | IOSTANDARD = LVCMOS33 | DRIVE = 8 | SLEW = FAST | PULLUP;
```

```
net "clk" LOC =v10 | IOSTANDARD = LVCMOS33 | period = 100MHz;
```

```
net "count[0]" LOC =P16 | IOSTANDARD = LVCMOS33 | DRIVE = 8 | SLEW = FAST;
```

```
net "count[1]" LOC =N15 | IOSTANDARD = LVCMOS33 | DRIVE = 8 | SLEW = FAST;
```

```
net "count[2]" LOC =N16 | IOSTANDARD = LVCMOS33 | DRIVE = 8 | SLEW = FAST;
```

```
net "count[3]" LOC =U17 | IOSTANDARD = LVCMOS33 | DRIVE = 8 | SLEW = FAST;
```

```
net "dp" LOC =B3 | IOSTANDARD = LVCMOS33 | DRIVE = 8 | SLEW = FAST;
```

```
net "dp" LOC =A5 | IOSTANDARD = LVCMOS33 | DRIVE = 8 | SLEW = FAST;
```

```
net "out[0]" LOC =C6 | IOSTANDARD = LVCMOS33 | DRIVE = 8 | SLEW = FAST;
```

```
net "out[1]" LOC =D6 | IOSTANDARD = LVCMOS33 | DRIVE = 8 | SLEW = FAST;
```

```
net "out[2]" LOC =C5 | IOSTANDARD = LVCMOS33 | DRIVE = 8 | SLEW = FAST;
```

```
net "out[3]" LOC =C4 | IOSTANDARD = LVCMOS33 | DRIVE = 8 | SLEW = FAST;
```

```
net "out[4]" LOC =A4 | IOSTANDARD = LVCMOS33 | DRIVE = 8 | SLEW = FAST;
```

```
net "out[5]" LOC =B4 | IOSTANDARD = LVCMOS33 | DRIVE = 8 | SLEW = FAST;
```

```
net "out[6]" LOC =A3 | IOSTANDARD = LVCMOS33 | DRIVE = 8 | SLEW = FAST;
```

TestBench:

```
module testbench;
    reg clk,rst;
    wire [6:0] out;
    wire dp;
    wire [3:0] count;

    Counter c1(clk,rst,dp,out,count);


    always
        #5 clk = ~clk;

    initial
    begin
        $display("RST  Count");
        clk = 0;
        rst = 0;
        #10
        rst = 1;
        $monitor("%b  %d",rst,count);
    end
endmodule
```

Output:

```
# RST  Count
# 1  0
# 1  1
# 1  2
# 1  3
# 1  4
# 1  5
# 1  6
# 1  7
# 1  8
# 1  9
# 1 10
# 1 11
# 1 12
# 1 13
# 1 14
# 1 15
```

Waveform:

 

Dataflow:

