

DIGITAL SYSTEM DESIGN LAB

LAB 1



Spring 2021

CSE308L DSD LAB

Submitted by: **Shah Raza**

Registration No. : **18PWCSE1658**

Class Section: **B**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Student Signature: _____

Submitted to:

Engr. Madiha Sher

Tuesday, April 20th, 2021

Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar

Task # 01:

Develop a program to control on Board LED using On board available switch.

Problem Analysis:

Truth Table:

Input	Output
0	0
1	1

Code:

Module:

```
module buff(O1,O2,O3,O4,O5,O6,O7,O8,I1,I2,I3,I4,I5,I6,I7,I8);
    input I1,I2,I3,I4,I5,I6,I7,I8;
    output O1,O2,O3,O4,O5,O6,O7,O8;

    buf (O1,I1);
    buf (O2,I2);
    buf (O3,I3);
    buf (O4,I4);
    buf (O5,I5);
    buf (O6,I6);
    buf (O7,I7);
    buf (O8,I8);
endmodule
```

Test Bench:

```
module testBuff;
    reg I1,I2,I3,I4,I5,I6,I7,I8;
    wire O1,O2,O3,O4,O5,O6,O7,O8;

    buff b(O1,O2,O3,O4,O5,O6,O7,O8,I1,I2,I3,I4,I5,I6,I7,I8);


    initial
    begin
        $monitor ("%b %b %b %b %b %b %b %b %b %b %b %b %b %b %b %b",I1,I2,I3,I4,I5,I6,I7,I8,O1,O2,O3,O4,O5,O6,O7,O8);
        I1=0;I2=0;I3=0;I4=0;I5=1;I6=1;I7=1;I8=1;
        #5
        I1=1;I2=1;I3=1;I4=1;I5=0;I6=0;I7=0;I8=0;
        #5
        I1=0;I2=0;I3=0;I4=0;I5=0;I6=0;I7=0;I8=0;
        #5
        I1=1;I2=1;I3=1;I4=1;I5=1;I6=1;I7=1;I8=1;
    end
endmodule
```

Output:


```
run
#0000111100001111
#1111000011110000
#0000000000000000
#1111111111111111
```

Waveform:


At 0ns:

 


At 5ns:

 


At 10ns:

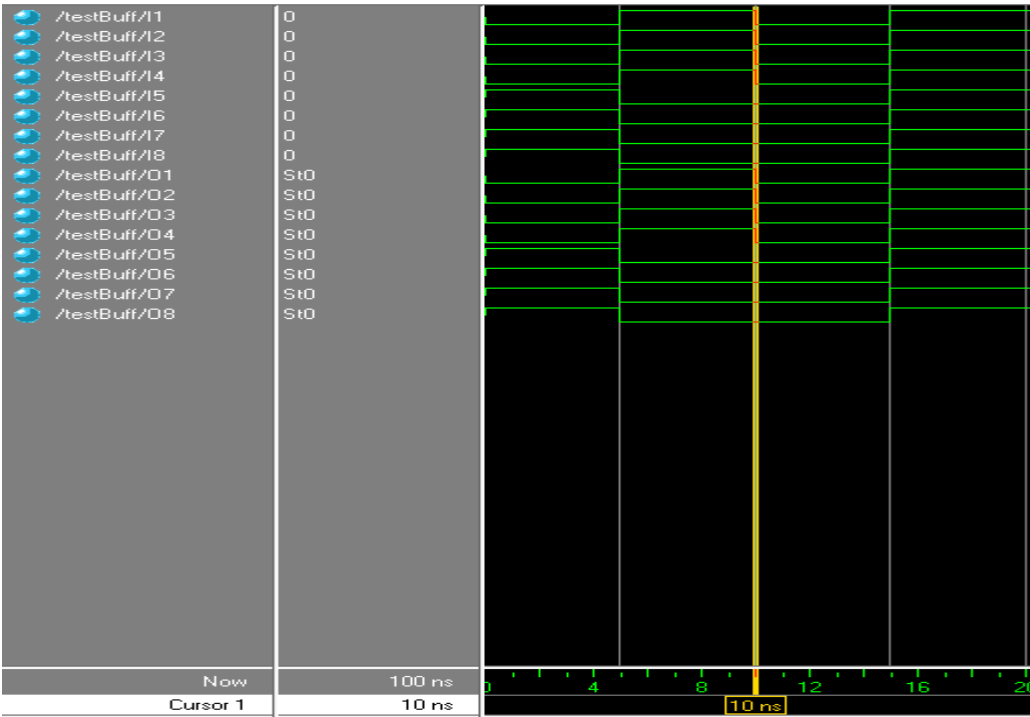

At 15ns:

 

Dataflow:

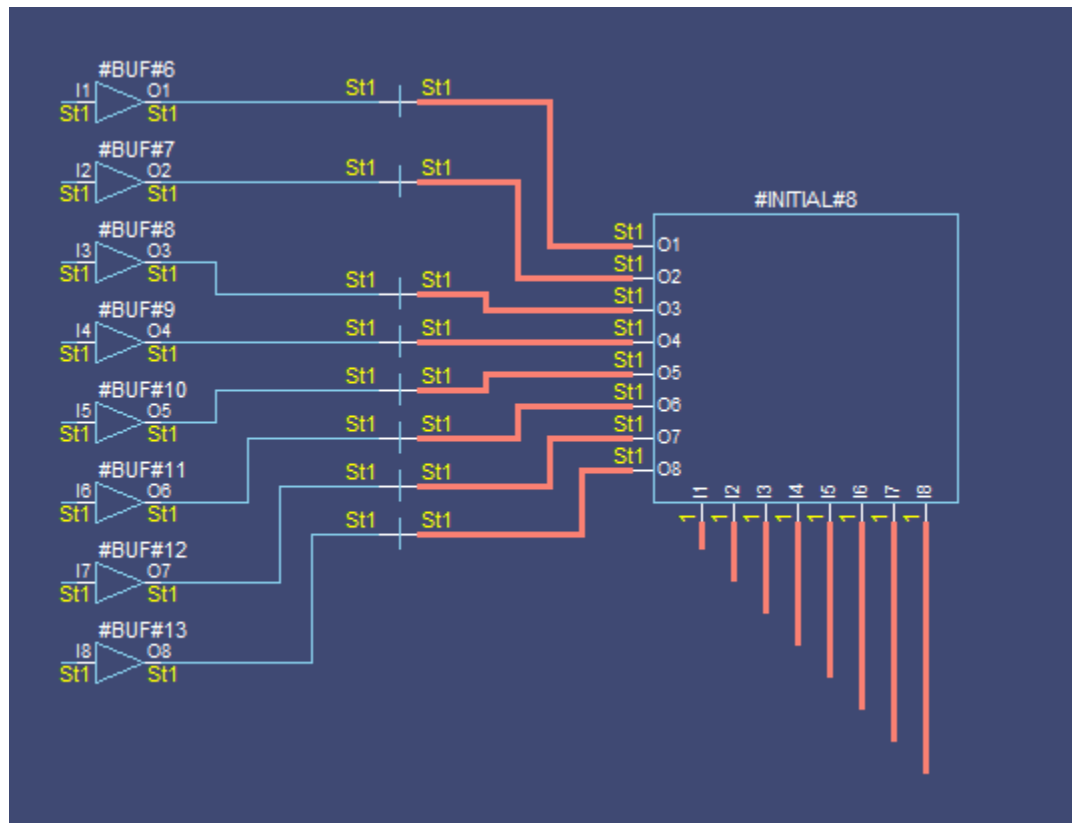

Task # 02:

Develop a program that implements a 2x1 multiplexer using gate level modeling.

Problem Analysis:**Truth Table:**

S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Simplified Expression for Z:

$$Z = (\overline{A.S}) + (B.S)$$

Code:**Module:**

```
module Mux2(Z,A,B,S);
    output Z;
    input A,B,S;

    wire So,X,Y;

    not (So,S);
    and (X,A,So);
    and (Y,B,S);
    or (Z,X,Y);
endmodule
```

Test Bench:

```
module testMux2x1;
    wire Z;
    reg A,B,S;
    Mux2 m(Z,A,B,S);

    initial
    begin
        $monitor ("%b %b %b %b",S,A,B,Z);
        A=0;B=0;S=0;
        #5
        A=0;B=1;S=0;
        #5
        A=1;B=0;S=0;
        #5
        A=1;B=1;S=0;
        #5


        A=0;B=0;S=1;
        #5
        A=0;B=1;S=1;
        #5
        A=1;B=0;S=1;
        #5
        A=1;B=1;S=1;
    end
endmodule
```

Output:


```
run
#0000
#0010
#0101
#0111
#1000
#1011
#1100
#1111
```


Waveform:


At 10ns:

 

At 30ns:

 

Dataflow:

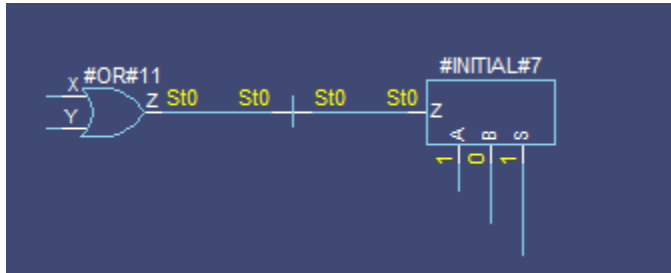

Task # 03:

Develop a program that implements a 4x1 multiplexer using gate level modeling.

Problem Analysis:

Truth Table:

S0	S1	A	B	C	D	Z
0	0	A	x	x	x	A
0	1	x	B	x	x	B
1	0	x	x	C	x	C
1	1	x	x	x	D	D

Simplified Expression for Z:

$$Z = (A.S0n.S1n) + (B.S0n.S1) + (C.S0.S1n) + (D.S0.S1)$$

Code:

Module:

```
module Mux4x1(Z,A,B,C,D,S0,S1);
    input A,B,C,D,S0,S1;
    output Z;
    wire S0n,S1n,V,W,X,Y;

    not (S0n,S0);
    not (S1n,S1);

    and (V,A,S0n,S1n);
    and (W,B,S0n,S1);
    and (X,C,S0,S1n);
    and (Y,D,S0,S1);

    or (Z,V,W,X,Y);
endmodule
```

Test Bench:

```
module testMux4x1;

    reg A,B,C,D,S0,S1;
    wire Z;

    Mux4x1 m4(Z,A,B,C,D,S0,S1);

    initial
    begin
        $monitor ("%b %b %b %b %b %b %b",S0,S1,A,B,C,D,Z);

        S0=0;S1=0;A=1;B=0;C=0;D=0;
        #5

        S0=0;S1=1;A=0;B=1;C=0;D=0;
        #5

        S0=1;S1=0;A=0;B=0;C=1;D=0;
        #5

        S0=1;S1=1;A=0;B=0;C=0;D=1;


    end

endmodule
```


Output:

```
run
#0010001
#0101001
#1000101
#1100011
```


Waveform:
At 0ns:

 


At 5ns:

 

At 10ns:

 

At 15ns:

 

Dataflow:

