

DIGITAL SYSTEM DESIGN LAB

LAB #04



Spring 2021

CSE308L DSD LAB

Submitted by: **Shah Raza**

Registration No. : **18PWCSE1658**

Class Section: **B**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Student Signature: _____

Submitted to:

Engr. Madiha Sher

Monday, May 10, 2021


Department of Computer Systems Engineering
University of Engineering and Technology, Peshawar

Objectives:

This lab will enable students to:

- Code using Behavioral level modeling
- Implement an 8 Bit Ring Counter

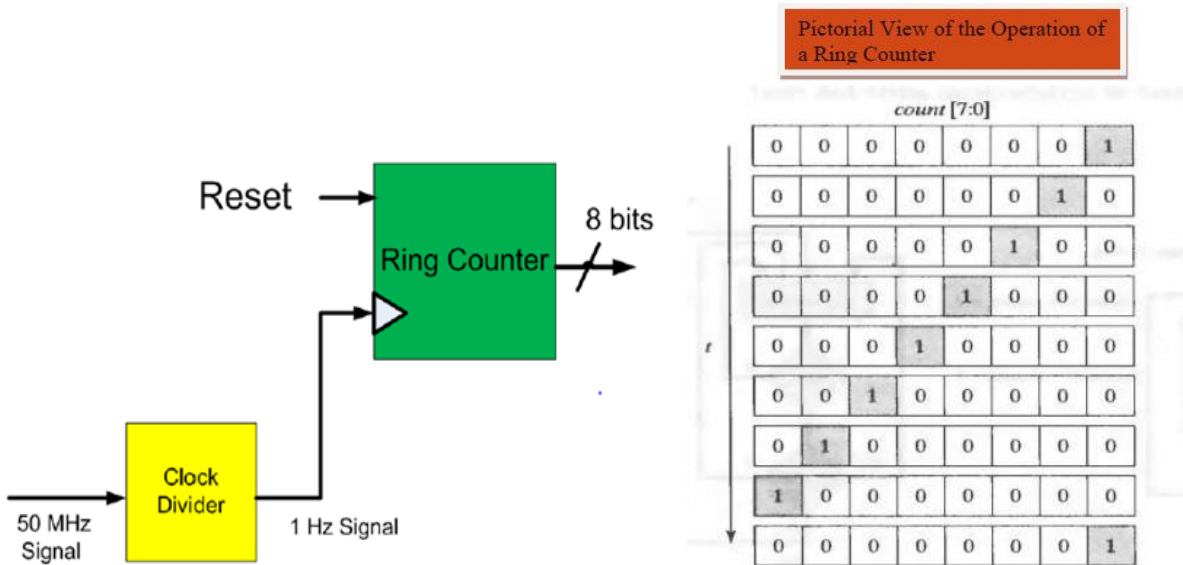Task # 01: Implementation of 8 bit Ring Counter.



Code:

Ring Counter:

```
module Counter_8bit(clock,reset,Output);
    input clock,reset;
    output [7:0] Output;

    reg [7:0] C;

    always @(posedge clock or reset)
        if(reset)
            C = 8'b00000001;
        else
            begin
                C <= C << 1;
                C[0] <= C[7];
            end
        assign Output = C;
endmodule
```


Test Bench:

```
module testCounter;
    reg clk, rst;
    wire [7:0] Out;

    Counter_8bit c1(clk,rst,Out);
    always
        #1 clk = ~clk;
    initial
    begin
        $display("Rst Out");
        clk = 0; rst = 1;
        $monitor("%b %b",rst,Out);
        #1 rst =1;
        #1 rst =0;
        #28 $stop;
    end
endmodule
```

Output:

```
# Rst Out
# 1 00000001
# 0 00000010
# 0 00000100
# 0 00001000
# 0 00010000
# 0 00100000
# 0 01000000
# 0 10000000
# 0 00000001
# 0 00000010
# 0 00000100
# 0 00001000
# 0 00010000
# 0 00100000
# 0 01000000
# 0 10000000
-- -- -- -- --
```

 Waveform:

Dataflow:

